

Class-D Audio Amplifier Using PWM (LTspice Simulation Report)

1. Project Overview

This project focuses on the design and simulation of a Class-D audio amplifier using the PWM (Pulse Width Modulation) technique. The circuit is designed and simulated in LTspice to demonstrate efficient audio amplification.

2. Working Principle

The audio signal is converted into a PWM signal by comparing it with a high-frequency carrier generated using an NE555 timer. The PWM drives a MOSFET, and an LC filter reconstructs the audio signal.


3. Circuit Explanation

The circuit consists of a carrier generator (NE555), comparator, MOSFET switching stage, LC low-pass filter, and an 8-ohm load.

4. Block Diagram

Name: Kunal Date: _____ Branch: Electronics

now block diagram

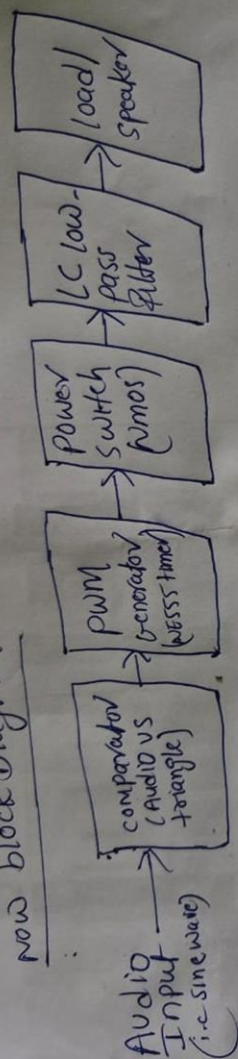

Kunal Dabe TheoryClass-D Amplifier -

A class-D amplifier is a high efficiency amplifier that uses pulse width modulation (PWM) instead of linear amplification.

In this method, the audio signal is converted into a PWM signal by comparing it with a high frequency carrier waveform.


In this circuit, the 555 timer is configured in astable mode to generate a high frequency triangular waveform.

The carrier signal is compared with low frequency audio signal using ideal comparator. The comparator output is a PWM signal whose duty cycle varies accordingly to audio amplitude.

The PWM signal drive MOS transistors operating as high-speed switch. The switching output contain high frequency component, which are removed using an LC ~~filter~~ low pass filter. This filtered output reconstructs the original audio signal across the load.


The class D amplifier offer high efficiency and low power dissipation also widely use

6.Circuit Diagram

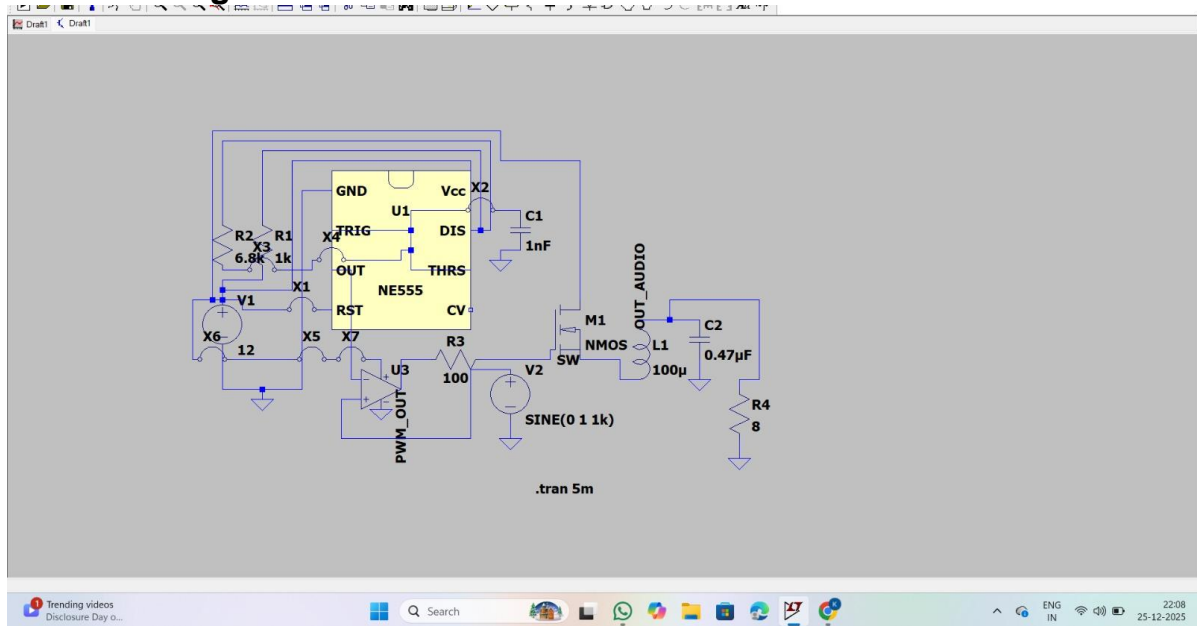

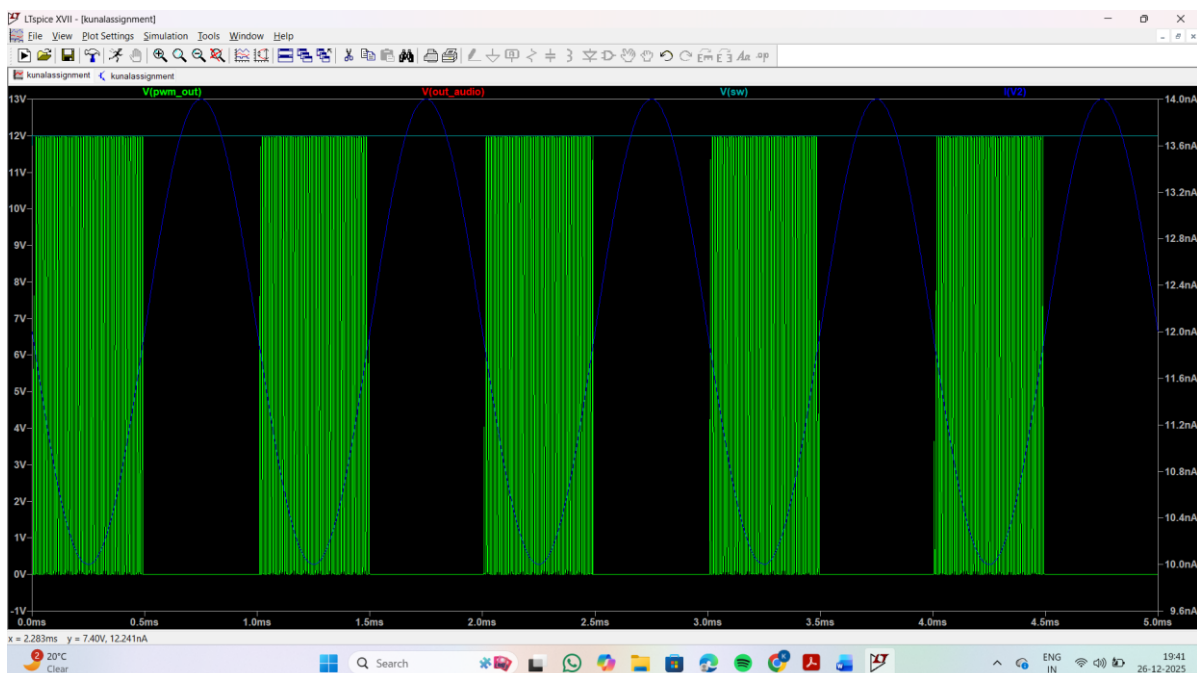7.Simulation Results

Simulation results show proper PWM generation, MOSFET switching, and smooth audio output after LC filtering.



8s.Conclusion

The Class-D amplifier was successfully simulated, demonstrating high efficiency audio amplification using PWM technique.